

CO Number	Course Outcome
CO1	To define basic laws, terminologies and theories pertaining to DC and AC (1-phase and 3-phase) electrical circuits.
CO2	Explain concepts of electrical circuits, the components of switchgear, transformers and electromechanical energy conversion devices and their applications.
CO3	Apply the concepts of transformers, AC & DC machines and energy consumption in solving real life numerical problems.
CO4	Analyze and examine different types of DC and AC electrical circuits (1-phase and 3-phase).

Time: 1.5 Hrs.

M. M. 20

Section A

Q1. Attempt all questions:

(1X5 = 5 Marks)

- Define average and rms value of an alternating quantity.
- Cite the difference between ideal and practical current source.
- Explain active and passive elements with the help of example?
- What is the significance of peak factor?
- What is the form factor of ac current $i = 400\sin(157t + \frac{\pi}{6})$?

CO1
CO1
CO2
CO1
CO2

Section B

Q2. Attempt all questions:

(2.5X4 = 10 Marks)

- a i) Use nodal analysis to calculate the currents in various resistors of the circuit shown in Fig.1 CO4

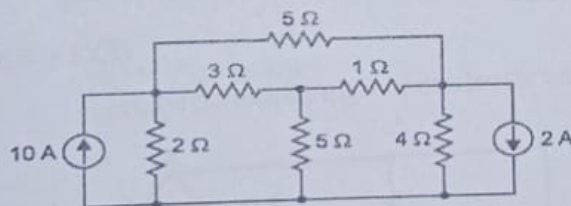


Fig.1

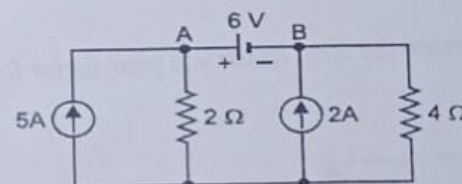


Fig.2

Or

- ii) Calculate current in the 4Ω resistor by mesh current method for the circuit shown in Fig.2 CO4
- b i) Calculate the value of V_{AB} in Fig.3 as shown below CO3

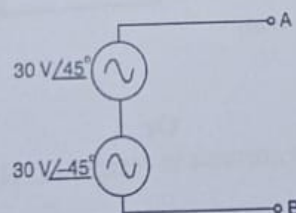


Fig.3

- ii) Use mesh current method to determine current I_x in the circuit shown in Fig.4.

Or

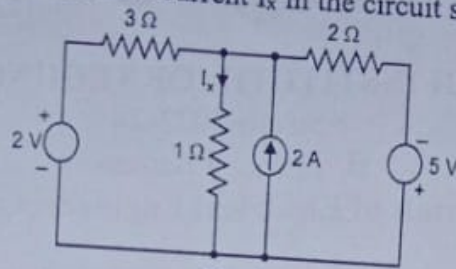


Fig.4

CO3

- c i) Find the current in 4Ω resistance of the circuit shown in Fig.5

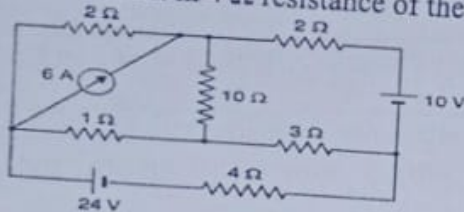


Fig.5

Or

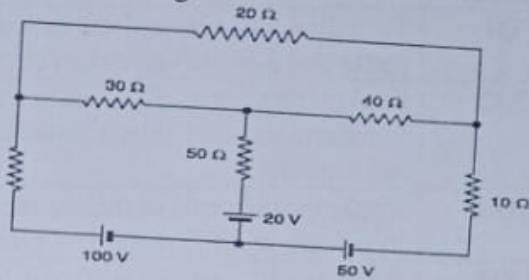


Fig.6

CO3

- ii) Find the current in 50Ω resistance using nodal analysis in Fig.6
d i) Find the average and rms value for the waveform shown in Fig.7

CO3

CO3

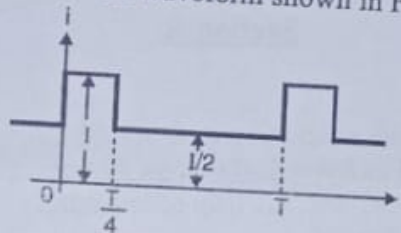


Fig.7

Or

- ii) The following four e.m.fs. act together in a circuit:
 $e_1 = 10 \sin \omega t$; $e_2 = 8 \sin(\omega t + \pi/3)$; $e_3 = 4 \sin(\omega t - \pi/6)$; $e_4 = 6 \sin(\omega t + 3\pi/4)$
Calculate the e.m.f. represented by $e_1 - e_2 + e_3 - e_4$.

CO3

Section C

Q3

(5X1 = 5 Marks)

- i) Determine the form factor and peak factor for the waveform in figure 8 shown below.

CO4

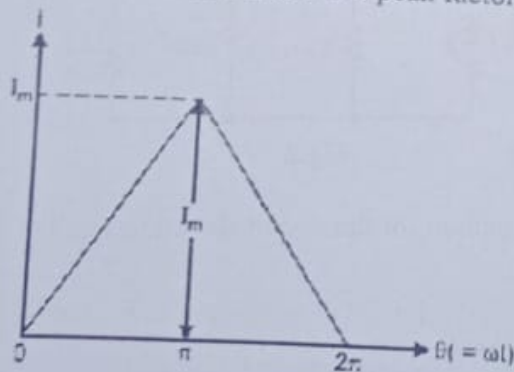


Fig.8

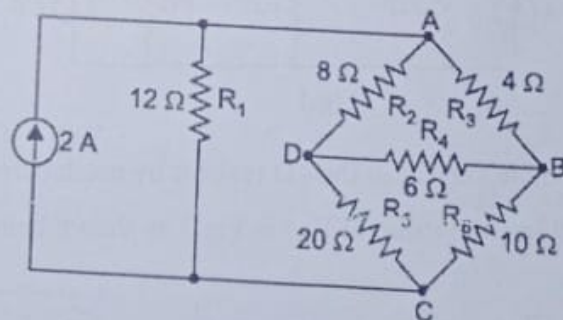


Fig.9

Or

- ii) Using mesh current method, calculate the currents in resistances R_3 , R_4 , R_5 and R_6 of the circuit shown in Fig.9

CO4