

R

1

M. M. 15

(1X3 = 3 Marks)

CO1

- 2

(2X4 = 8 Marks)

CO2

- CO2

CO4


- CO4

Or

- $$I_{ma} = 150 \times 10^{-3} \text{ A}$$

- c i) Find the average and rms values of the ac voltage whose waveform is given below.

CO4

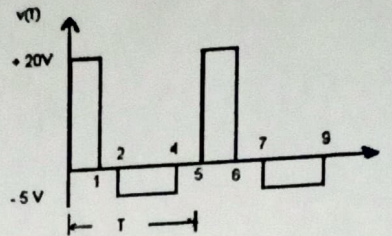

Or

- ii) A resistance and inductance are connected in series across voltage $v = 283 \sin 314t$. The current expression is found to be $4 \sin (314t - \pi/4)$. Find the values of resistance, inductance and power factor.
- d i) Illustrate the relationship between line and phase voltages and currents for a Delta-connected 3-phase balanced system.

CO4

CO3

Or

- ii) Illustrate various types of magnetic materials. Also, explain ferrites and its types.

CO3


Section C

Q3. Attempts all the questions.

1x4=4 Marks

- i) A current of 5A flows through a non-inductive resistance connected in series with a choking coil when a voltage of 230V, 50 Hz is applied across it. If the voltage across the resistance is 115V and that across choking coil is 184V, calculate (a) resistance, reactance and impedance of the coil, (b) the power absorbed by the coil and (c) the total power.

CO4

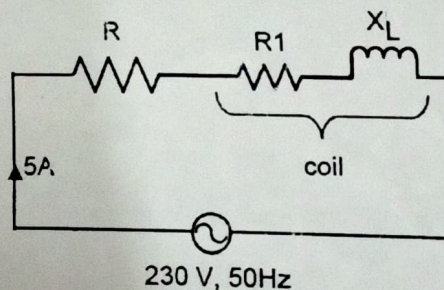

Or

- ii) A 46 mH inductive coil has resistance of 10Ω . How much current will it draw, if connected across 100 V, 50 Hz source? Also, determine the value of capacitance that must be connected across the coil to make the power factor of the circuit be unity.

CO4