

B. Tech. First Semester
Basic Electrical Engineering (KEE-101T)

CO Number	Course Outcome (Please include all COs of your Course here)
CO1	To define [L1: Knowledge] basic laws, terminologies and theories pertaining to DC and AC (1-phase and 3-phase) electrical circuits.
CO2	Explain [L2: Comprehension] concepts of electrical circuits, the components of low voltage electrical installations, transformers and electromechanical energy conversion devices and their applications.
CO3	Apply [L3: Application] the concepts of transformers, AC & DC machines and energy consumption in solving real life numerical problems.
CO4	Analyze [L4: Analysis] and examine different types of DC and AC electrical circuits (1-phase and 3-phase).

Time: 1.5 Hrs.

Section A

M. M. 15

(1X3 = 3 Marks)

Q1. Attempt all questions:

- a) Draw the volt ampere characteristics of an ideal and practical voltage source. CO1
- b) Define linear and nonlinear circuits. CO1
- c) List the various types of sources used in electrical circuits. CO1

Section B

(2X4 = 8 Marks)

Q2. Attempt all questions:

- a i) Find the current in $6\text{ k}\Omega$ resistor in Fig. 1. by converting the current source to a voltage source. CO2

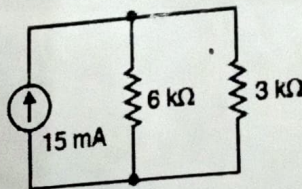


Fig. 1

Or

- ii) Two coils connected in series have a resistance of $18\ \Omega$ and when connected in parallel have a resistance of $4\ \Omega$. Find the value of resistances. CO2
- b i) Using mesh analysis, calculate the voltage drop across the $1\text{ k}\Omega$ resistor in the circuit shown in Fig. 2. CO4

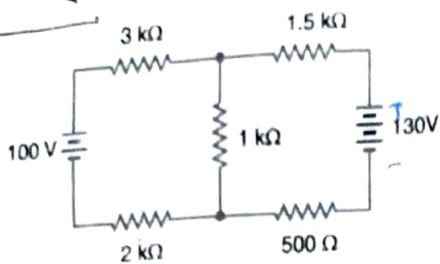


Fig. 2

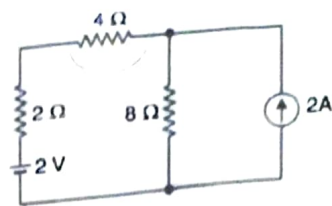


Fig. 3

- ii) Use nodal analysis to calculate the voltage across and current through 4Ω resistor in the circuit shown in Fig. 3. CO4

- c i) Using superposition principle, calculate the current through 10Ω resistor in the circuit shown in Fig. 4. CO4

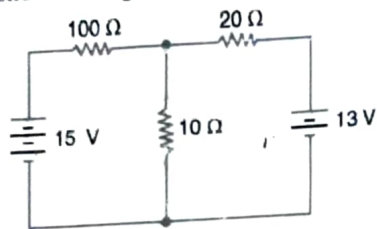


Fig. 4

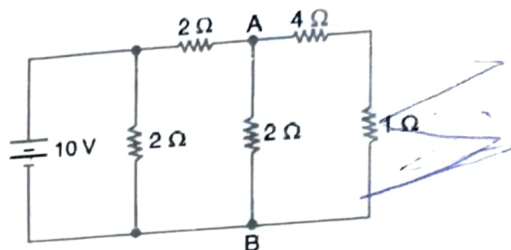


Fig. 5

- ii) Using Thevenin's theorem, calculate the potential difference across branch AB of the network shown in Fig. 5. CO4
- d i) Using delta/star transformation, calculate the resistance between terminals A and C of the network shown in Fig. 6. CO3

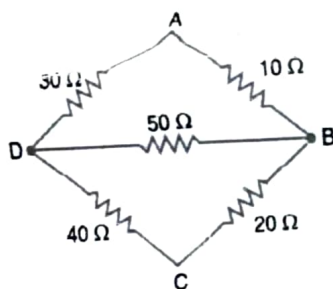


Fig. 6

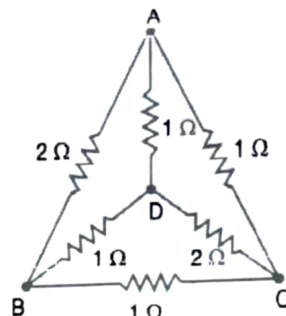


Fig. 7

- ii) In the network shown in Fig. 7, calculate the resistance between terminals B and C using star/delta transformation. CO3

Section C

Q3. Attempt all the questions.

(4X1 = 4 Marks)

- i) Using Thevenin's theorem, calculate the current through the resistor $R = 1\Omega$ of the network shown in Fig. 8. CO4

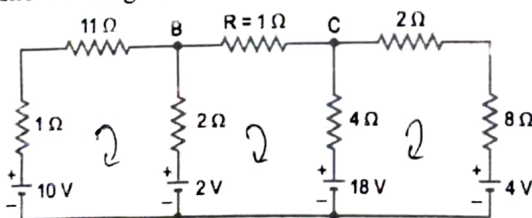


Fig. 8

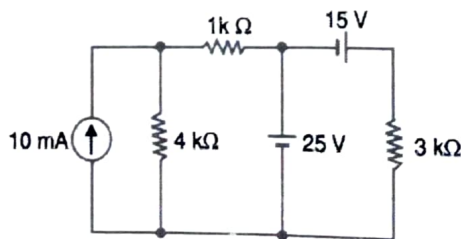


Fig. 9

- ii) Using superposition principle, calculate the voltage across $4k\Omega$ resistor in Fig. 9. CO4